

Introduction

Daytime running lights (DRLs) are now widely seen in modern vehicles. Most designs are designed with a 555 timer and reference op amps to generate a pulse width modulation (PWM) and to detect faults. Both of these functions can be replaced with a single TPLD1202 device, in turn saving board space and costs, and simplifying designs.

PWM Dimming

The reference design [Automotive Daytime Running Light \(DRL\) LED Driver Reference Design with Linear Thermal Foldback](#) utilizes a 555 timer to help generate a PWM signal to dim the LEDs. Instead of using an external device, the TPLD1202 features a PWM generator with adjustable duty cycle and frequencies. The duty cycle is modified using counter data, calculated by $\text{Duty cycle (\%)} = (\text{DATA}/256) \times 100$. This ranges from a minimum of 0% to 99.61% duty cycle percentage.

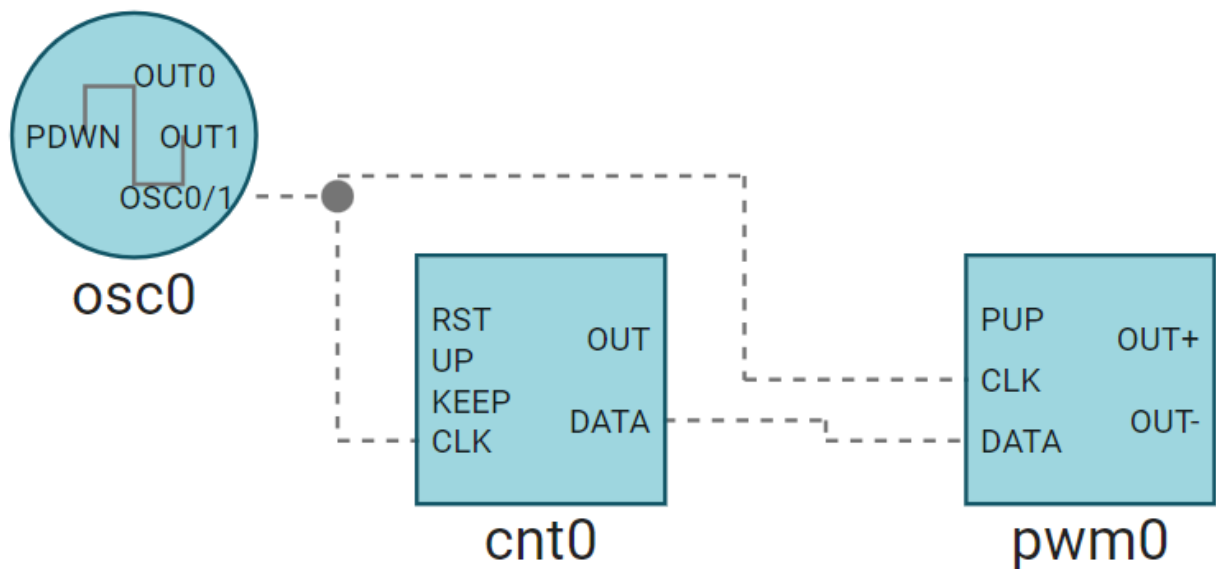


Figure 1. PWM Generator Block

For a detailed description of the PWM generator featured in TPLD1202-Q1, please refer to the applications brief [PWM Generators in TI Programmable Logic Devices](#).

Fault Detection

Detecting a fault in an LED string is as simple as monitoring the MOSFET drain voltage. For more information, please refer to the two-part Technical Article:

- [Designing Daytime Running Lights, Part 1: Adding One-fail-all-fail LED Fault Detection](#)
- [Designing Daytime Running Lights, Part 2: Responding to an LED Fault](#)

As a summary, there are four different possible faults that can be detected in different ways:

- LED short in mirror string
 - $V_{\text{drain}} = (2 \times V_f) + (I_{\text{mirror}} \times R_0)$
- LED short in reference string
 - $V_{\text{drain}} = I_{\text{mirror}} \times R_0$
- Open circuit in mirror string
 - $V_{\text{drain}} = 0V$
- Open circuit in reference string
 - V_{drain} oscillations

Functional operation of the LED string results in $V_{\text{drain,normal}} = V_f + (I_{\text{mirror}} \times R_0)$. We can see that the first three fault states result in a voltage higher or lower than $V_{\text{drain,normal}}$. A fault detector can be implemented with a window comparator, with an upper limit of 110% and lower limit of 90% of $V_{\text{drain,normal}}$. When V_{drain} is within 90-110% of $V_{\text{drain,normal}}$, the comparator outputs high, otherwise outputting low.

The fourth fault state can be difficult to detect as the oscillations make the output of the comparator pulse repeatedly. This is solved by latching the output of the window comparator the first time the voltage exits the “good” window.

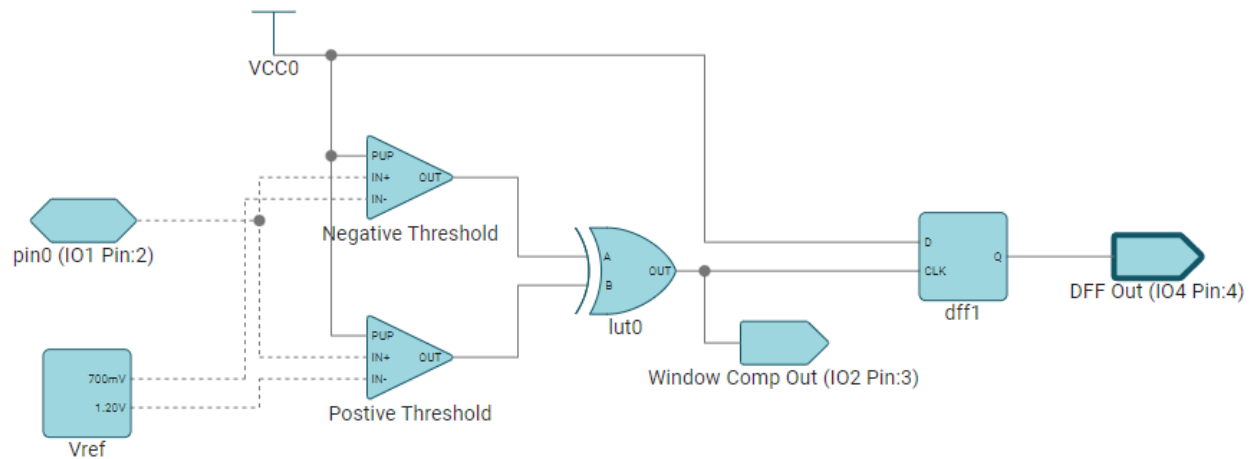


Figure 2. Fault Detection Implementation

The original design in [Designing Daytime Running Lights, Part 2: Responding to an LED Fault](#) is a minimum two device implementation that can be replaced by one TPLD. This, in addition to utilizing the TPLD PWM generator results in one TPLD1202 replacing 3+ devices.

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2025, Texas Instruments Incorporated

Last updated 10/2025