

# Overview of 3.3V Controller Area Network (CAN) Transceivers



Jason Blackman and Scott Monroe

## ABSTRACT

3.3V Controller Area Network (CAN) transceivers offer advantages and flexibility with respect to 5V CAN transceivers while being compatible and interoperable with each other. Power consumption is lower with 3.3V transceiver compared with 5V transceivers. There is potential for power supply simplification and cost savings when the microprocessor communicating with the transceiver is also at 3.3V. This application note explains these advantages and the devices in TI's CAN transceiver portfolio that can be used for 3.3V CAN systems.

## Table of Contents

<b>1 Theory of Operation</b> .....	2
<b>2 Measurements Demonstrating Operation</b> .....	3
<b>3 Conformance Testing</b> .....	7
<b>4 3.3V Device Advantages</b> .....	7
<b>5 Summary</b> .....	7
<b>6 References</b> .....	7
<b>7 Revision History</b> .....	8

## List of Figures

Figure 1-1. Typical CAN Network.....	2
Figure 1-2. Typical CAN Bus Levels for 5V and 3.3V Transceivers.....	2
Figure 2-1. Waveforms of Two 5V SN65HVD255 Transceivers.....	3
Figure 2-2. Waveforms of Two 3.3V SN65HVD234 Transceivers.....	4
Figure 2-3. Waveform of Two SN65HVD255 Transceivers, One With a +1V Ground Shift.....	4
Figure 2-4. Waveform of Two 5V SN65HVD255 Transceivers With Split Termination, One With a +1V Ground Shift.....	5
Figure 2-5. Single Termination (left) and Split Termination (right).....	5
Figure 2-6. Waveform of a 5V SN65HVD255 and a 3.3V SN65HVD234.....	6
Figure 2-7. Bus Communication of a 5V SN65HVD1050 and a 3.3V SN65HVD230.....	6

## List of Tables


Table 4-1. Chart of Supply Current for Three Different Two-Node Buses.....	7
--	---

## Trademarks

All trademarks are the property of their respective owners.

## 1 Theory of Operation

The ISO 11898 specification details the physical layer requirements for CAN bus communications. CAN is a low-level communication protocol over a twisted pair cable, similar to RS-485

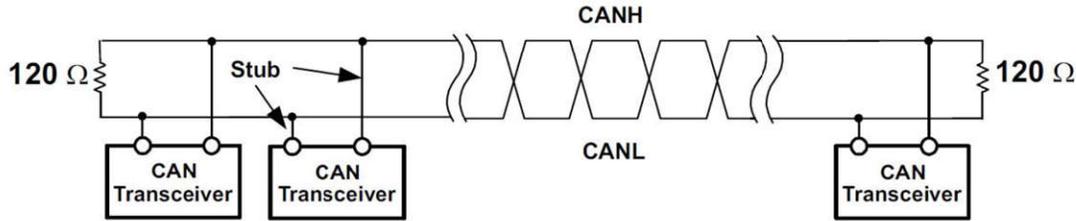


**Figure 1-1. Typical CAN Network**

An important feature of CAN is that the bus is not actively driven during logic 'High' transmission, referred to as 'recessive.' During this time, both bus lines are typically at the same voltage, approximately  $V_{CC} / 2$ . The bus is only driven during 'dominant' transmission, or during logic 'Low.' In Dominant, the bus lines are driven such that  $(CANH - CANL) \geq 1.5V$ . This allows a node transmitting a 'High' to detect if another node is trying to send a 'Low' at the same time. This is used for non-destructive arbitration, where nodes start each message with an address (priority code) to determine which node gets to use the bus. The node with the lowest binary address wins arbitration and continues with its message. There is no need to back-off and retransmit like other protocols.

CAN receivers measure differential voltage on the bus to determine the bus level. Since 3.3V transceivers generate the same differential voltage ( $\geq 1.5V$ ) as 5V transceivers, all transceivers on the bus (regardless of supply voltage) can decipher the message. In fact, the other transceivers cannot tell there if anything is different about the differential voltage levels.

Figure 1-2 shows bus voltages for 5V transceivers as well as 3.3V transceivers. For 5V CAN, CANH and CANL are weakly biased at about 2.5V ( $V_{CC} / 2$ ) during recessive. The recessive common-mode voltage for 3.3V CAN is biased higher than  $V_{CC} / 2$ , typically about 2.3V. This is done to better match the common mode point of the 5V CAN transceivers and minimize the common mode changes on the bus between 3.3V and 5V transceivers. Since CAN was defined as a differential bus with wide common mode allowing for ground shifts (DC offsets between nodes) this isn't needed for operation, but minimizes emissions in a mixed network. In addition, by using split termination to filter the common mode of the network a significant reduction in emissions is possible. The ISO 11898-2 standard states that transceivers must operate with a common-mode range of -2V to 7V, so the typical 0.2V common-mode shift between 3.3V and 5V transceivers doesn't pose a problem.

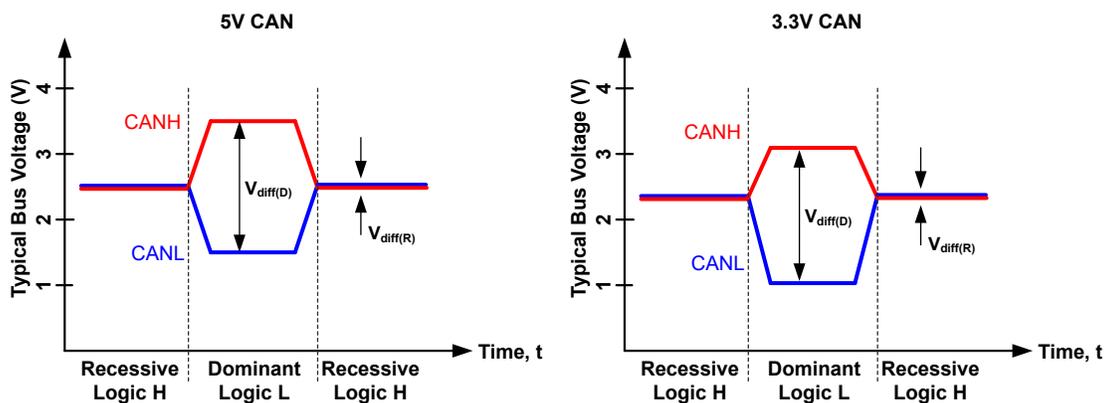

**Figure 1-2. Typical CAN Bus Levels for 5V and 3.3V Transceivers**

Previously, 3.3V CAN transceivers were not used for automotive applications because they cannot meet strict EMC requirements required by major automotive manufacturers. This application note references legacy 3.3V CAN family such as SN65HVD23x, which were not approved for use in heterogeneous automotive networks. TI's new generation of automotive 3.3V CAN transceivers, TCAN3403-Q1 and TCAN3404-Q1, overcome this challenge and pass IEC 62228-3:2019 under both homogeneous and heterogeneous network conditions. For more detailed information, see [How Automotive-Qualified Electromagnetic-Compliant 3.3V CAN FD Transceivers Improve ECU Performance](#).

## 2 Measurements Demonstrating Operation

Figure 2-1 shows two 5V transceivers communicating on the same bus. In this case, transceiver (XCVR) 1 and 2 are both Texas Instruments' SN65HVD255 CAN transceiver. The signals 'TXD1' and 'TXD2' show what each transceiver is driving onto the bus, while 'RXD1' and 'RXD2' show what each transceiver is reading from the bus. The two upper signals are the bus lines, CANH (yellow) and CANL (light blue). The red waveform below them is the calculated differential voltage between CANH and CANL.



**Figure 2-1. Waveforms of Two 5V SN65HVD255 Transceivers**

A simplified bit pattern was used to demonstrate CAN bus principles.

- Bit time 1: one transceiver transmits a dominant bit while the other remains recessive.
- Bit time 2: both transceivers are recessive.
- Bit time 3: both transmit dominant, showing what can happen during arbitration.

As shown, the differential voltage is slightly greater when both transceivers are dominant due to the output transistors of each transceiver being in parallel, resulting in a smaller voltage drop and greater differential voltage output.

Figure 2-2 shows the same setup but with two 3.3V transceivers (TI SN65HVD234). The differential voltage between the bus lines during dominant bits is lower than the 5V devices that were tested, but is still meets the requirements of the ISO 11898-2 standard. In addition, the minimum differential bus voltage for the 5V devices is the same as with the 3.3V devices (1.5V). This means that designers have no advantage if choosing 5V devices for their higher differential driving abilities, since it is not specified that the differential output is higher.

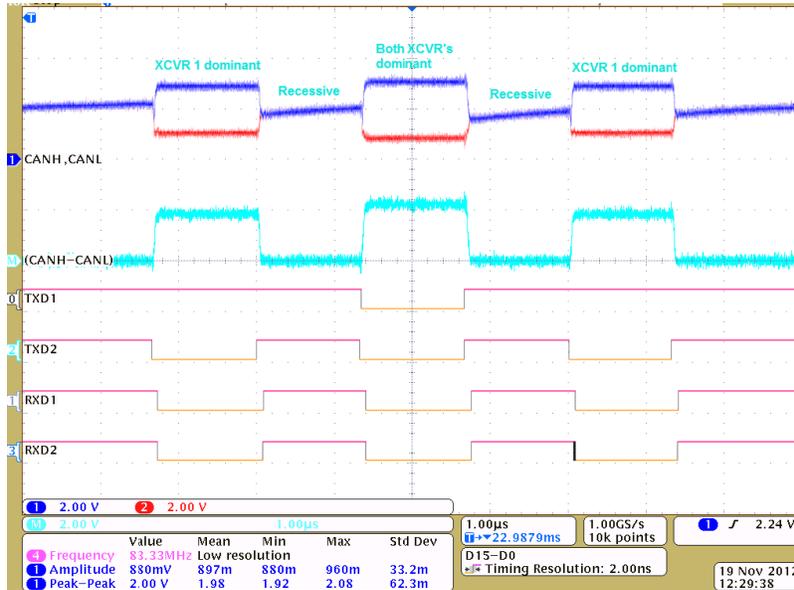


Figure 2-2. Waveforms of Two 3.3V SN65HVD234 Transceivers

Figure 2-3 shows how robust CAN is with common mode differences. The red Math signal shows the common mode voltage instead of differential voltage in previous plots. The bus signals become very ugly when arbitration between ground shifted transceivers occurs. However, the RXD1 signal shows that the transceivers don't have a problem because the differential signal is good and the transceiver correctly detects the signal on the bus.

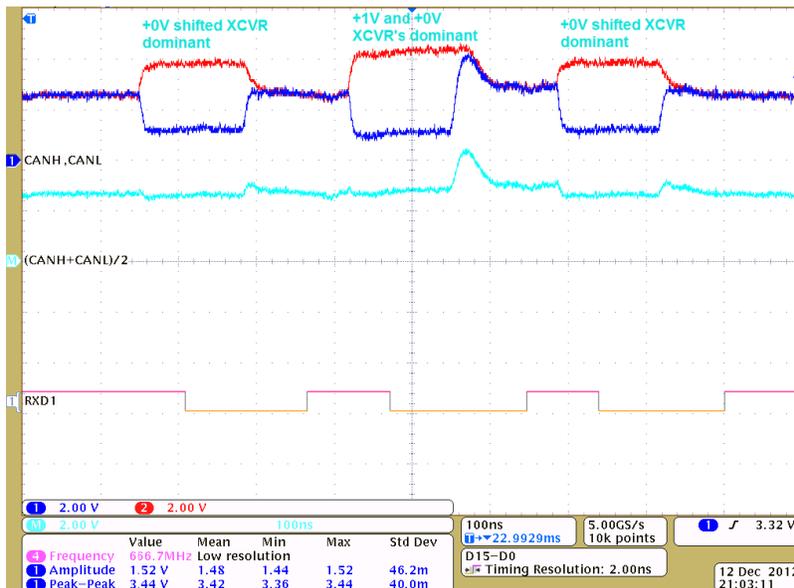


Figure 2-3. Waveform of Two SN65HVD255 Transceivers, One With a +1V Ground Shift

Figure 2-4 shows the same situation as the previous figure, now with split termination instead of traditional single termination. Split termination, shown in Figure 2-4, helps filter out high frequency noise that can occur when there are ground potential differences between nodes. The setup for Figure 2-4 used a  $C_L$  of 4.7nF, which is typical.

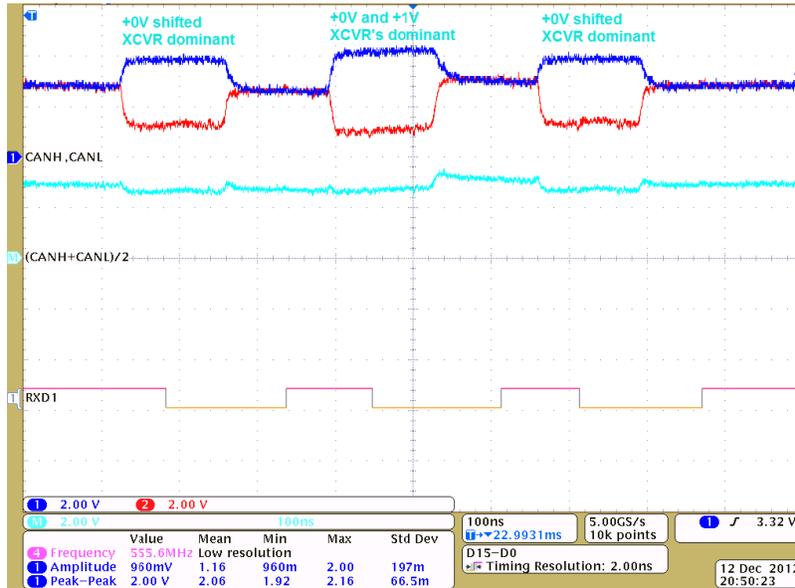


Figure 2-4. Waveform of Two 5V SN65HVD255 Transceivers With Split Termination, One With a +1V Ground Shift

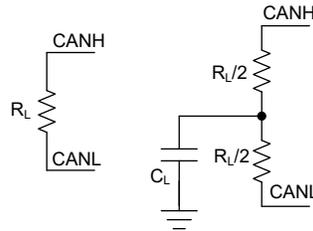


Figure 2-5. Single Termination (left) and Split Termination (right)

Figure 2-6 shows communication with a mixed network of one 3.3V transceiver and one 5V transceiver. As before, the digital signals TXD1, TXD2, RXD1 and RXD2 show that both transceivers are accurately talking to each other and there is little common mode shift during the communication in contrast to the 5V homogeneous network with a 1V ground shift.

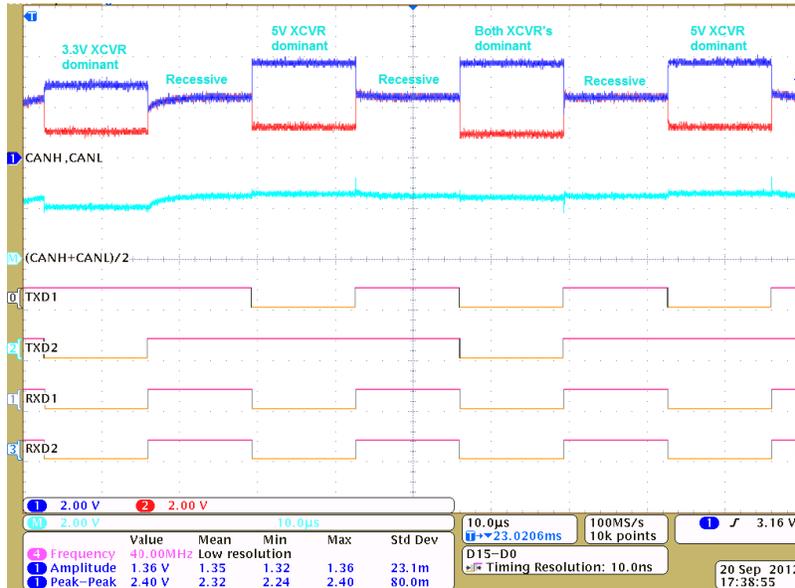


Figure 2-6. Waveform of a 5V SN65HVD255 and a 3.3V SN65HVD234

Figure 2-7 shows a CAN frame in a mixed network of two 3.3V transceivers and one 5V transceiver to demonstrate these principles in a CAN frame from a functional mixed system.



Figure 2-7. Bus Communication of a 5V SN65HVD1050 and a 3.3V SN65HVD230

### 3 Conformance Testing

The TI SN65HVD23x 3.3V CAN families have been successfully tested by the internationally recognized third party communications and systems (C&S) group GmbH to the GIFT/ICT CAN High-Speed Transceiver Conformance Test. This testing covers a homogeneous network of all 3.3V transceivers and a heterogeneous network where four out of sixteen CAN nodes are the 3.3V transceiver and the remaining twelve CAN nodes are a mix of three other “golden” reference, non TI 5V CAN transceivers. Both TI 3.3V CAN transceiver families successfully passed this testing with no findings and the certificates of authentication were issued.

### 4 3.3V Device Advantages

The 3.3V transceivers tested clearly operate in mixed supply networks, which provides advantages. The first advantage is lower power. Not only are 3.3V transceivers lower voltage, they are also lower current.

Table 4-1 shows the supply current for 3.3V devices is reduced by nearly half. Combined with the already lower supply voltage, this results in significant power reduction.

**Table 4-1. Chart of Supply Current for Three Different Two-Node Buses**

Case1: 2X SN65HVD234	SN65HVD234#1 ICC(mA)	SN65HVD234#1 ICC(mA)
Both recessive	7.1	7.2
#1 dominant	38.4	7.2
Both dominant	25.9	26.1
Case2: 2X SN65HVD255	SN65HVD255#1 ICC(mA)	SN65HVD255#1 ICC(mA)
Both recessive	18.6	18.6
#1 dominant	61.8	18.4
Both dominant	44.6	44.8
Case3: Mixed	SN65HVD234 ICC(mA)	SN65HVD255 ICC(mA)
Both recessive	7.2	18.6
SN65HVD234 dominant	38.6	18.6
SN65HVD255 dominant	7.2	61.8
Both dominant	11.7	58.9

Several other advantages emerge when used with a 3.3V microcontroller. The digital I/O of a 5V transceiver would be level shifted either externally or in the 5V CAN transceiver to avoid damaging the microcontroller (unless it is 5V tolerant) whereas, a 3.3V transceiver could be directly connected to this microcontroller. The SN65HVD233/234/235 3.3V transceivers have 5V tolerant inputs so they may be used directly with a 3.3V or a 5V microcontroller. If 5V was only used in the system for CAN, a 3.3V CAN transceiver would eliminate the need for the 5V power supply, simplifying the power domains and lowering the cost.

### 5 Summary

3.3V and 5V CAN transceivers are interoperable because the high-speed CAN physical layer uses differential signaling that is the same for a 3.3V and 5V CAN transceiver. In addition, both the 3.3V and 5V CAN transceivers have the same wide common mode range accommodating not only the typical signaling but also providing wide margin for ground shift potential. For systems that can benefit from the advantages of 3.3V transceivers, such as simplified power supplies and lower power consumption, they offer clear advantages in their use either in a homogeneous 3.3V CAN network or in a mixed 3.3V and 5V CAN network.

### 6 References

- [How Automotive-Qualified Electromagnetic-Compliant 3.3V CAN FD Transceivers Improve ECU Performance](#)

## 7 Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from Revision * (January 2023) to Revision A (May 2025)</b>	<b>Page</b>
• Added information that the newer 3.3V transceivers are available in <a href="#">Section 1</a> .....	<a href="#">2</a>

---

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2025, Texas Instruments Incorporated